SE-IOT: Internet of Things



Working with Binary Signals

Derek Kiong dkiong@nus.edu.sg





© 2016-2018 NUS. The contents contained in this document may not be reproduced in any form or by any means, without the written permission of ISS, NUS other than for the purpose for which it has been supplied

ATA/SE-IOT/04 GPIO.v3.ppt

Working with Binary Outcomes





GPIO Module

 RPi.GPIO module allows working with GPIO devices

import RPi.GPIO as GPIO

- Pin numbering mode
 - Board number

GPIO.setmode(GPIO.BOARD)


- Broadcom SOC channel designation GPIO.setmode (GPIO.BCM)
- Set warnings

GPIO. setwarnings (False)





GPIO.BOARD VS GPIO.BCM

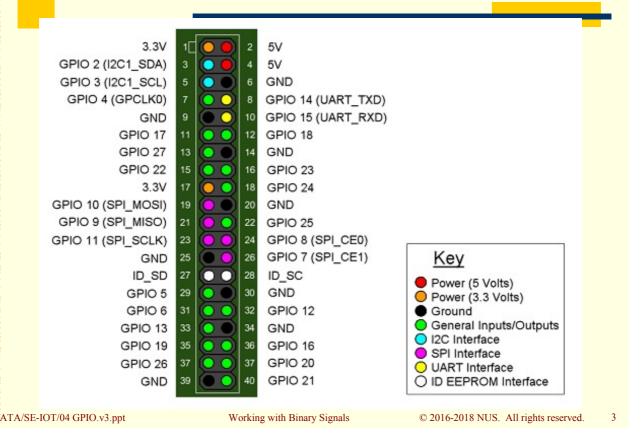

GPIO operations (output)


- Output modeGPIO.setup(pin, GPIO.OUT)
- ◆ Bring pin low □low potential at pin GPIO.output (pin, GPIO.LOW)
- ◆ Bring pin high □high potential at pin GPIO.output (pin, GPIO.HIGH)
 - may test via LED and limiting resistor in series






LED connection

 LED with 240 ohms limiting resistor

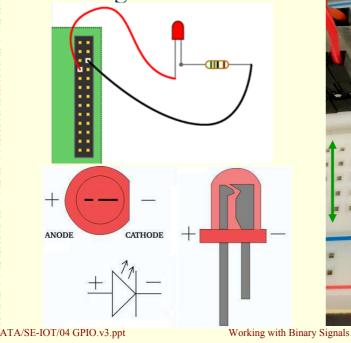

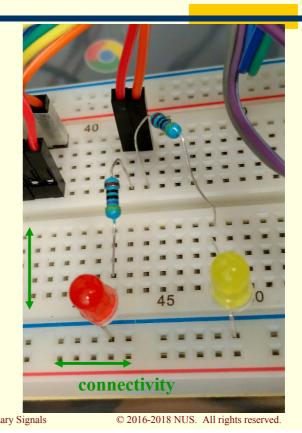

ISS

Wiring 4 channel Relay

entropy of the control of the contro	
Relay pins	RP pins
GND	6 (ground)
IN1	15 (GPIO 22)
IN2	16 (GPIO 23)
IN3	18 (GPIO 24)
IN4	22 (GPIO 25)
VCC	2 (+ve)





Operating 4-channel Relay

```
import RPi.GPIO as GPIO
  import sys
  GPIO.setmode(GPIO.BCM)
  GPIO.setwarnings(False)
  pinList = [22,23,24,25]
  if len(sys.argv)>2:
       [cmd, lamp, state] = sys.argv
       lamp = int(lamp) # which lamp?
       state = int(state) # off/on?
       GPIO.setup(pinList[lamp], GPIO.OUT)
       GPIO.output (pinList[lamp],
                     (GPIO.HIGH if state == 0 else GPIO.LOW))
  else:
       print "Usage: %s <relay> <0/1>" % sys.argv[0]
ATA/SE-IOT/04 GPIO.v3.ppt
                          Working with Binary Signals
                                               © 2016-2018 NUS. All rights reserved.
```

National University of Singapore



Operating 4-channel Relay

```
$ python relay.py 0 1
                         # turns IN1 on
$ python relay.py 0 0
                         # turns IN1 off
$ python relay.py 1 1
                         # turns IN2 on
$ python relay.py 1 0
                         # turns IN2 off
$ python relay.py 2 1
                         # turns IN3 on
$ python relay.py 2 0
                         # turns IN3 off
$ python relay.py 3 1
                         # turns IN4 on
$ python relay.py 3 0
                         # turns IN4 off
```





Encapsulate Relay device

```
import RPi.GPIO as GPIO
import sys

class Relay:
    def __init__(self):
        GPIO.setmode(GPIO.BCM)
        GPIO.setwarnings(False)
        self.pinList = [22,23,24,25]

def switch(self, lamp, state):
    pin = self.pinList[lamp]
    GPIO.setup(pin, GPIO.OUT)
    GPIO.output(pin,
        (GPIO.HIGH if state == 0 else GPIO.LOW))
```

ATA/SE-IOT/04 GPIO.v3.ppt

Working with Binary Signals

© 2016-2018 NUS. All rights reserved.

9

Using/Testing Relay class

```
def main():
    if len(sys.argv) > 2:
        [cmd,lamp,state] = sys.argv
        lamp = int(lamp)  # which lamp?
        state = int(state) # off/on?
        relay = Relay()
        relay.switch(lamp, state)
    else:
        print "Usage: %s <relay> <0/1>" % sys.argv[0]

if __name__ == "__main__":
    main()
```





GPIO operations (input)

- Input mode
 GPIO.setup(pin, GPIO.IN)
- Read pin (after setting low/high potential at pin)


GPIO.input(pin)


ATA/SE-IOT/04 GPIO.v3.ppt

Working with Binary Signals

 $\ensuremath{\mathbb{C}}$ 2016-2018 NUS. All rights reserved.

1

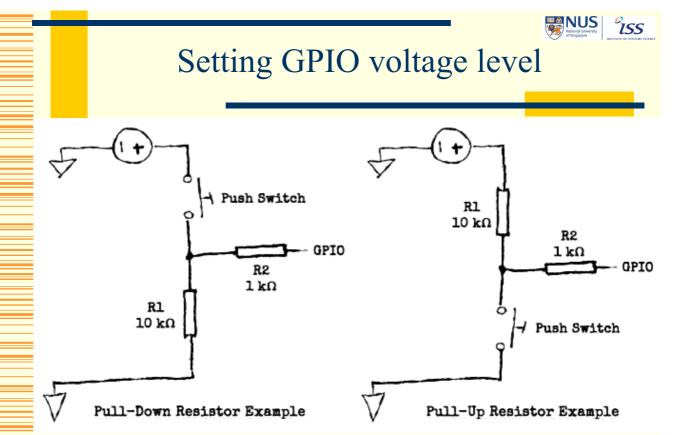

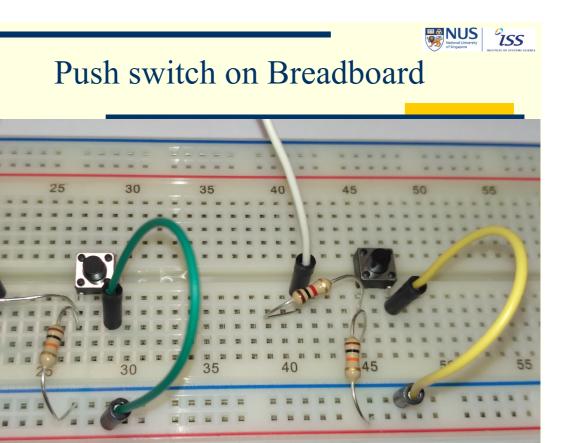

10kΩ □brown,black,orange 1kΩ □brown,black,red

ATA/SE-IOT/04 GPIO.v3.ppt

Working with Binary Signals

© 2016-2018 NUS. All rights reserved.

13

ISS

Wiring Switch GPIO

Switch setup pins	RP pins
VCC	2 (+ve)
OUT	11 (GPIO 17)
GND	6 (ground)





Encapsulating Switch (or Sensor)

```
import RPi.GPIO as GPIO
import time

class Switch:
    def __init__(self, pin):
        self.pin = pin
        GPIO.setmode(GPIO.BCM)
        GPIO.setwarnings(False)
        GPIO.setup(self.pin, GPIO.IN)

def getState(self):
    return GPIO.input(self.pin)
```

ATA/SE-IOT/04 GPIO.v3.ppt

Working with Binary Signals

© 2016-2018 NUS. All rights reserved.

14

Using/Testing Switch class





Edge detection

```
import RPi.GPIO as GPIO
import time
class Switch:
    def __init__(self, pin):
        self.pin = pin
        GPIO.setmode(GPIO.BCM)
        GPIO.setwarnings(False)
        GPIO.setup(self.pin, GPIO.IN)
    def getState(self):
        return GPIO.input(self.pin)
    def waitFor(self, event):
        GPIO.wait_for_edge(self.pin, event)
```

ATA/SE-IOT/04 GPIO.v3.ppt

Working with Binary Signals

© 2016-2018 NUS. All rights reserved.

Using/Testing Sensor class

```
def main():
    sw = Switch(17)
    state = sw.getState()
    while True:
        sw.waitFor(GPIO.RISING);
        print "Sensor is %d" % (sw.getState(),)
        sw.waitFor(GPIO.FALLING);
        print "Sensor is %d" % (sw.getState(),)
if __name__ == "__main__":
    main()
```





Event-driven

class Switch:

ATA/SE-IOT/04 GPIO.v3.ppt

Working with Binary Signals

© 2016-2018 NUS. All rights reserved.

10





Using Event-driven via subclassing

```
class SwitchEvent(Switch):
```





Summary

- Relay may turn on/off variety of equipment
 - Turn on lights/air-conditioner/heater
 - Turn on alarm
 - Release door lock
- Sensor output is binary 0/1 representing binary state
 - Open window
 - Broken lamp
 - Over-heating, dangerous pressure

ATA/SE-IOT/04 GPIO.v3.ppt

Working with Binary Signals

© 2016-2018 NUS. All rights reserved.